

How do I control a screen by using the 306-0007 relay box with only one output from the control system:

Regarding products:



306-0007: 2 relay box with power supply



302-0001, 307-0001, 307-0002, 310-0001, 310-0002, 310-0010: Control systems

How do I control a screen by using the 306-0007 relay box with only one output from the control system:

Neets do NOT recommend that you only control the screen by using 1 output, you have great risk of burning the relay in the relay box (destroy the relay). If you observe a “hanging relay” you might get it going again by giving it a light knock with a screwdriver or equal, be very careful and ALWAYS disconnect power before you try.

If you have no other options than only use one relay for the screen here is the way of getting it to do so:

You connect the screen to the “screen terminal” (RE-1, RE-2, N and earth) as you normally would do when using two relays. Remember to keep the 5 Amp fuse in (marked as “screen”)

After that connect RE-2 (in the connector named “CONTROL”) to GND in the same connector.

Now you can control up and down by connecting RE-1 (in the connector named “CONTROL”) to GND or not

Good luck with your new relay box

Best Regards

Neets